

# Analog IC Design – Cadence Tools

## Lab 09 (Mini Project 01)

### Two-Stage Miller OTA

-Two-stage Miller-compensated OTA Design:





Required specs:

Technology	0.13um	0.18um
Supply voltage	1.2V	1.8V
Static gain error	$\leq 0.05\%$	$\leq 0.05\%$
CMRR @ DC	$\geq 74\text{dB}$	$\geq 74\text{dB}$
Phase margin (avoid pole-zero doublets)	$\geq 70^\circ$	$\geq 70^\circ$
OTA current consumption	$\leq 60\mu\text{A}$	$\leq 60\mu\text{A}$
CMIR – high	$\geq 0.6\text{V}$	$\geq 1\text{V}$
CMIR – low	$\leq 0.2\text{V}$	$\leq 0.2\text{V}$
Output swing	0.2 – 1V	0.2 – 1.6V
Load	5pF	5pF
Buffer closed loop rise time (10% to 90%)	$\leq 70\text{ns}$	$\leq 70\text{ns}$
Slew rate (SR)	$5\text{V}/\mu\text{s}$	$5\text{V}/\mu\text{s}$





Activ  
Go to

1-Design Charts:





1-Input Pair M1,2:

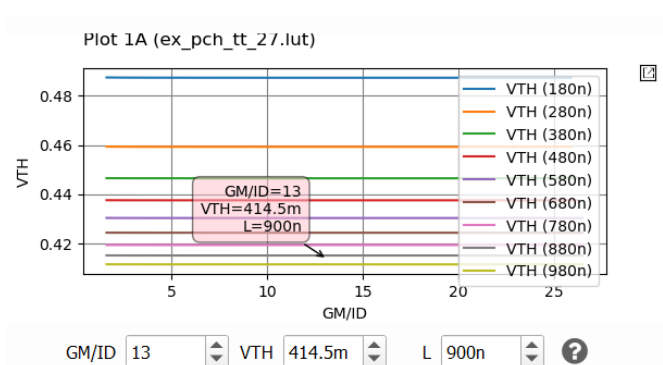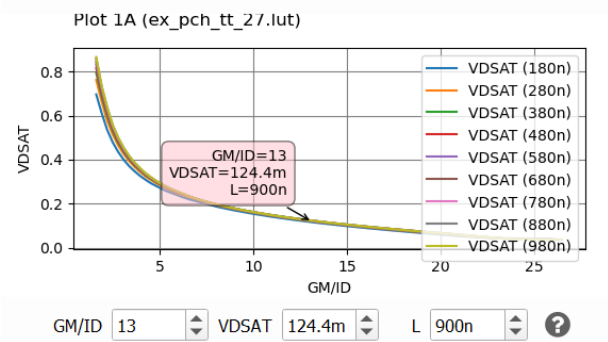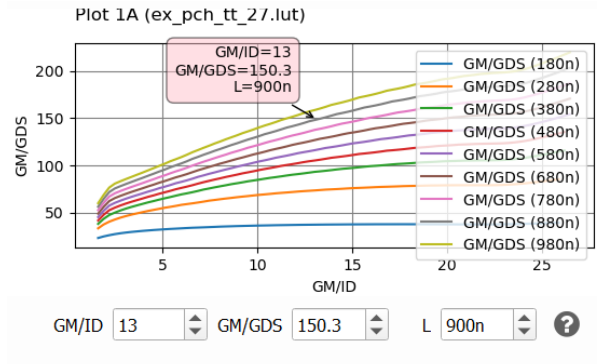 





2-Current mirror load M3,4:

   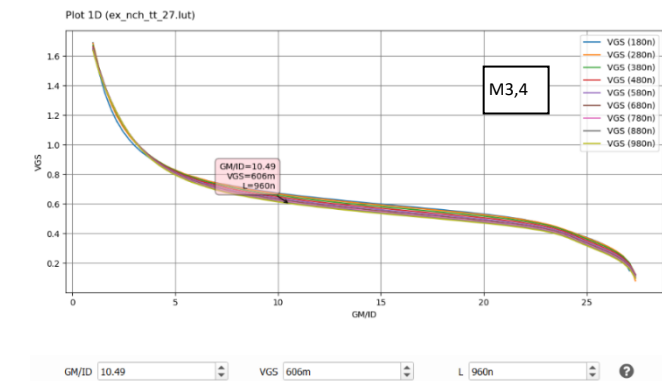
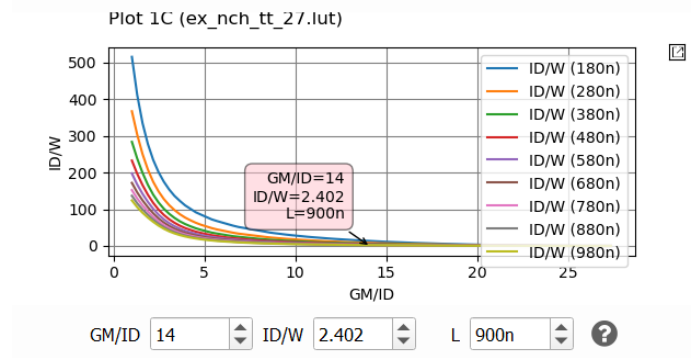   
### 3-Input transistor of second stage M5:



### 4-Tail current source M6,7:

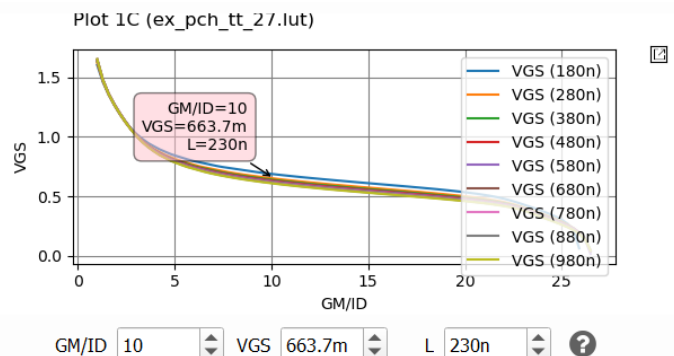 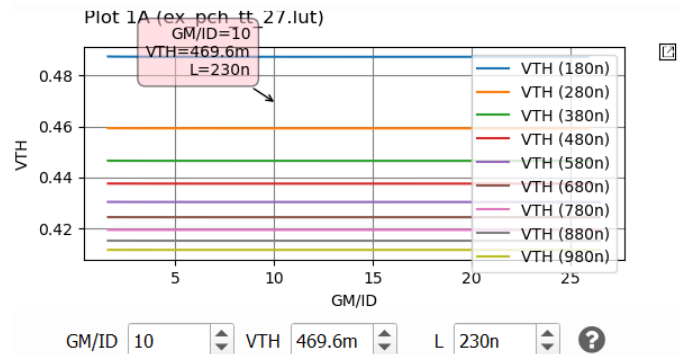 

Reporting the following:

1-Detailed design procedure and hand analysis:

-We use PMOS input pair as the CMIR is close to VDD and that reachable by PMOS

Design procedure:

$$1- \quad trise = 2.2 * taw \leq 70ns$$

$$Taw \leq 3.18 * 10^{-8} = 1/wu$$

$$Wu = \frac{gm1}{Cc} \geq 31.42Mrad$$

$$gm1,2 \geq 78.57$$

$$2- \quad slewrate = \frac{IB1}{Cc} = 5 \frac{v}{us}, \quad Cc = 2.5pf, \quad IB1 \leq 12.5uA, \quad IB2 \leq 47.5uA$$

$$3- \quad \left(\frac{gm}{ID}\right)_{1,2} \geq 12.57$$

$$4- \quad Acl = \frac{Aol}{1+BAol} = \frac{Aol+1-1}{1+Aol} = 1 - \frac{1}{Aol}$$

$$SGE = \frac{1}{LG} = Aol, \quad Aol \geq 2000, \quad Aol \geq 66dB$$

5- Assume the first stage gain is twice that of the second stage:

$$Av1 \geq 36dB \geq 63.095, \quad Av2 \geq 30dB \geq 31.622$$

$$\left(\frac{gm}{gds}\right)_{1,2} \geq 126.19, \quad \text{From Chart } \left(\frac{gm}{ID}\right)_{1,2} = 13, \quad L1,2 = 900n$$

$$\text{From Chart, } \frac{ID}{W} = 733.6m, \quad ID1 = 6.25uA, \quad W1,2 = 8.5um$$

$$6- \quad \text{Assume } \left(\frac{gm}{ID}\right)_{3,4} = 15, \quad gds1,2,3,4 = .628us, \quad \frac{gds}{ID} = 100m$$

$$\text{From chart, } L3,4 = 1.4um$$

$$7- \quad PM \geq 70, \quad \text{assume } wp2 = 4wu, \quad \frac{GM2}{Cl} = \frac{4GM1}{Cc},$$

$$gm5 = 650us, \quad \left(\frac{gm}{ID}\right)_{5min} = 13.68$$

8-

$$CMIR_{High} \geq 1v$$

$$1 \geq -|V_{gs1}| + V_{dsat7} + V_{DD}$$

$$1 \geq 1.8 - .56 - |V_{dsat7}|$$

$$V_{dsat7max} = 240mv = V *$$

$$\text{From Chart, } \frac{gm}{ID}{}_{6,7min} = 8.3, \quad \left(\frac{gm}{ID}\right)_{6,7} = 10$$

$$9- \quad CMRR \geq 74dB = Av_{ddB} - Av_{CMdB}, \quad Av_{CM} \leq -38dB, \quad .0125 \geq \frac{g_{ds6}}{2 * gm_{3,4}}$$

$$g_{ds6} \leq 2us, \quad \frac{gm}{g_{ds}}{}_{6,7} \geq 62.5, \quad \text{From chart, } L_{6,7} = 280n$$

$$10- \quad \left(\frac{gm}{g_{ds}}\right)_7 = 31.64, \quad gm_7 = 475us, \quad g_{ds7} = 15us$$

$$11- \quad Av_2 = gm_5(ro_5 || ro_7) = gm_5 \left( \frac{1}{g_{ds5} + g_{ds7}} \right) \geq 31.62$$

$$g_{ds5} \leq 5.55, \quad \left(\frac{gm}{g_{ds}}\right)_5 \geq 117.11 \quad \text{From Chart, } L_5 = 900n$$

$$12- \quad \left(\frac{gm}{ID}\right)_5 = 14, \quad \left(\frac{gm}{g_{ds}}\right)_5 = 119.3, \quad L_5 = 900n \quad \text{From Chart, } V_{GS5} = 553.1m$$

$$\text{From chart, } \left(\frac{ID}{W}\right)_5 = 2.4, \quad W_5 = 19.79um$$

$$13- \quad V_{GS3,4} = V_{GS5} = 553.1mv, \quad L_{3,4} = 1.4um, \quad \text{From chart } \left(\frac{gm}{ID}\right)_{3,4} = 12.86$$

$$\text{From Chart, } \left(\frac{ID}{w}\right)_{3,4} = 1.885, \quad W_{3,4} = 3.3um$$

14-CMIR<sub>Low</sub> verify:

$$.2 \geq -|V_{GS1}| + V * 1 + V_{GS3}$$

$$V_{GS3max} = 606mv, \quad \text{From chart, } \left(\frac{gm}{ID}\right)_{3,4min} = 10.49$$

$$\text{Verified, } \left(\frac{gm}{ID}\right)_{3,4} = 12.86$$

15-Peak to Peak output swing verification:

$$V_{outmin} = 0.2, \quad \left(\frac{gm}{ID}\right) 5 = 14, \quad V * 5 = .142mv < V_{outmin}$$

$$V_{outmax} = 1.6v, \quad \left(\frac{gm}{ID}\right) 7 = 10, \quad V * 7 = 0.2 = V_{outmax}$$

$$16-W_z = \frac{1}{Cc(\frac{1}{GM2-RZ})}, \quad \text{to throw zero to infinity,} \quad R_z = \frac{1}{GM2} = \frac{1}{gm5} = 1.538Kohm$$



17-We tuned after simulation to  $Cc = 2.3pF$  to get UGF spec

And  $W_{3,4} = 3.1um$ ,  $W_6 = 1.7um$ ,  $W_7 = 6.4um$ ,  $W_8 = 1.44um$  to tune the tail current.

	W	L	gm	ID	gm/ID	Vdsat	Vov	V*
M0,M1 Input pair	5.519um	900nm	81.25us	6.25uA	13	124.4mv	146mv	153mv
M3,M4 Current mirror	3.1um	1.4um	80.37us	6.25uA	12.86	125mv	407mv	155mv
M6,7 Tail current	W6=6.52um W7=6.4um	280nm	gm6=122us gm7=472us	ID6=12.2uA ID7=47.2uA	10	188mv	146mv	200mv
2 <sup>nd</sup> stage input M5	19.79um	900n	660.8	47.2uA	14	115.1mv	194.1mv	142mv

## PART 3: Open-Loop OTA Simulation:
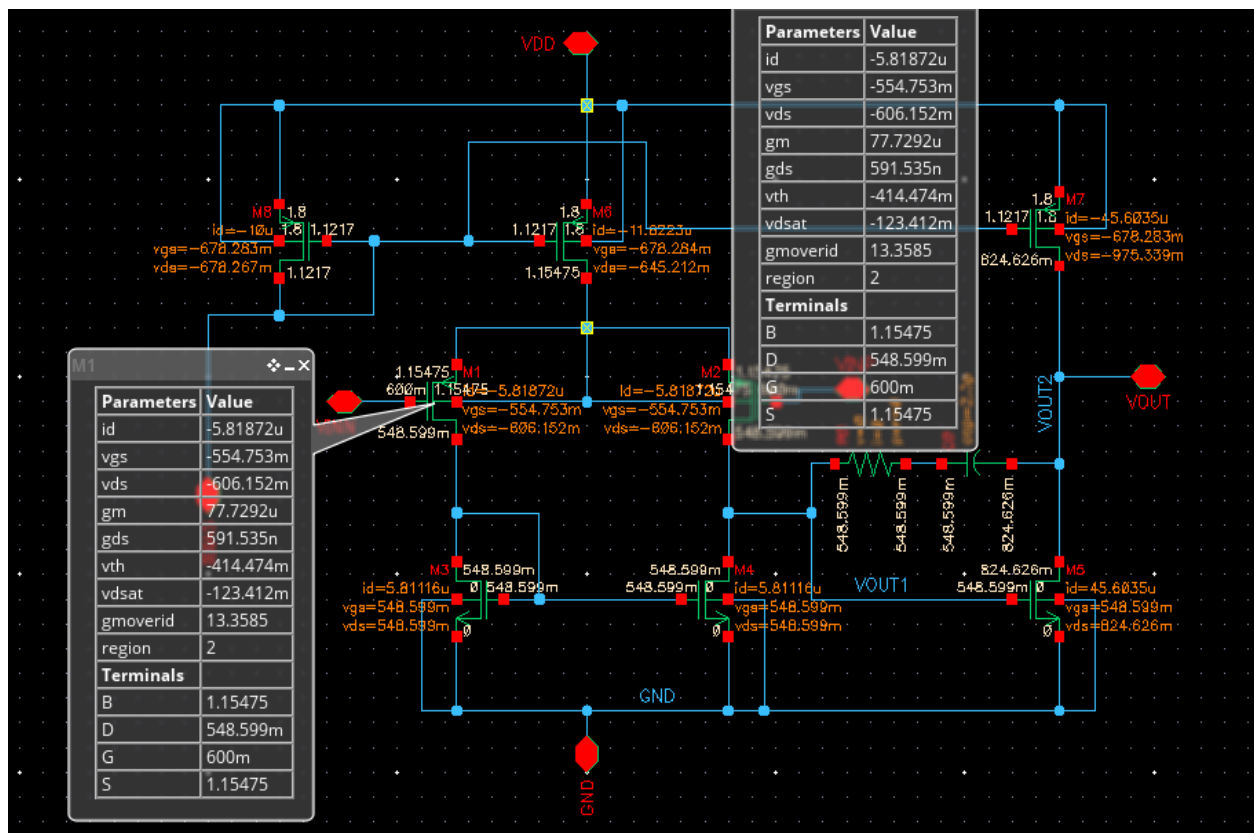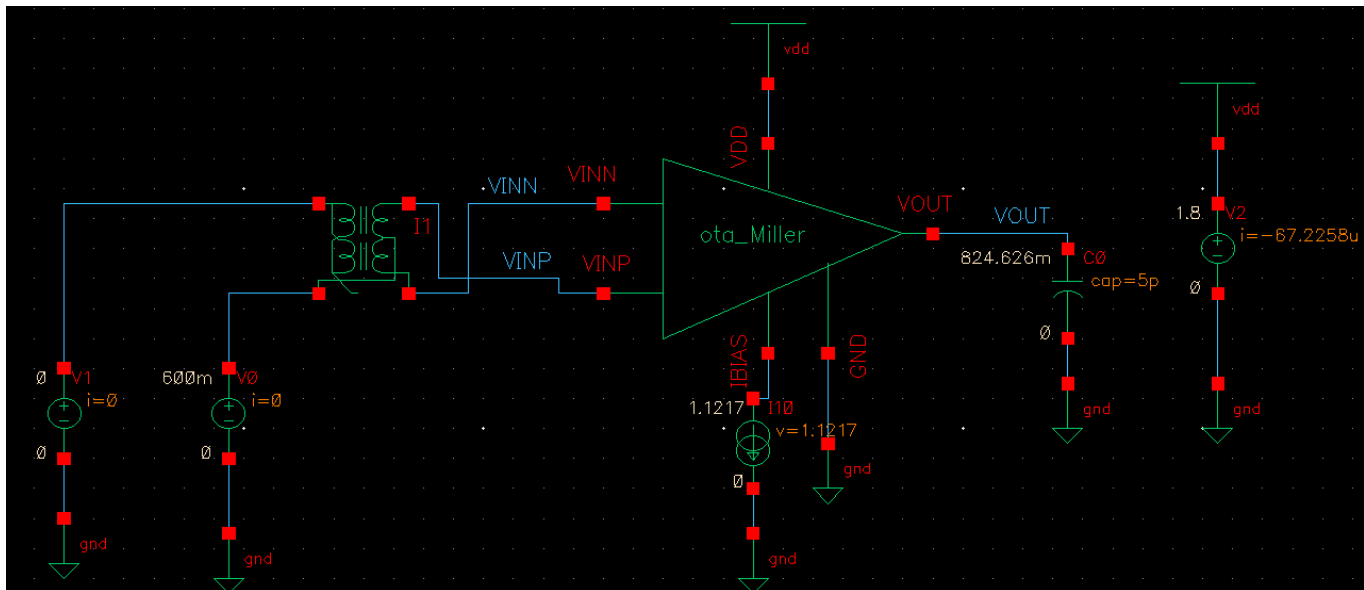
### 1-Schematic of the OTA and bias circuit with DC node voltages clearly annotated:



-Yes, The current (and gm) in the input pair exactly equal.


-VOUT1 = 548.59mv, because at CMInput Vout follows the mirror node Vf that equal to  

$$VOUT1 = Vf = VDD - VDS6 - VDS1 = 1.8 - .645 - .606 \approx 549mv$$

-VOUT2=691.64mv, because at CMInput:

$$VOUT2 = VDD - VDS7 = 1.8 - .975 = 825mv$$

## 1) Diff small signal ccs:

 

Output	Nominal	Spec
VOUT		
dB20(VF("VOUT"))		
bandwidth(VF("VOUT") 3 "lo...	1.973k	
unityGainFreq(VF("VOUT"))	5.161M	
gainBwProd(VF("VOUT"))	5.302M	

Hand analysis:

$$A_{vd} = A_{v1} * A_{v2} = (g_{m1}(r_{o2} || r_{o4})) * (g_{m5}(r_{o5} || r_{o7})) = 68.8 * 50.7$$

$$A_{vd} = 3488.16 = 70.1dB$$


$$BW = \frac{1}{R_{out1}g_{m5}R_{out2}C_c} = 1.8K$$

$$GBW = UGF = A_{vd} * BW = 5.5M$$

	simulation	analysis
A <sub>vd</sub>	68.5dB	70.1dB
BW	1.9K	1.8K
W <sub>u</sub>	5.161M	5.5M
GBW	5.3M	5.5M




## 2) CM small signal ccs:

 


$$A_{vCM} = -\frac{1}{2g_{m3} * r_{o6}} * A_{v2} = -1.5 = -3.8B$$

	Simulation	Analysis
$A_{vCM}$	-4.2dB	-3.8dB

## 3) (Optional) CMRR:

 
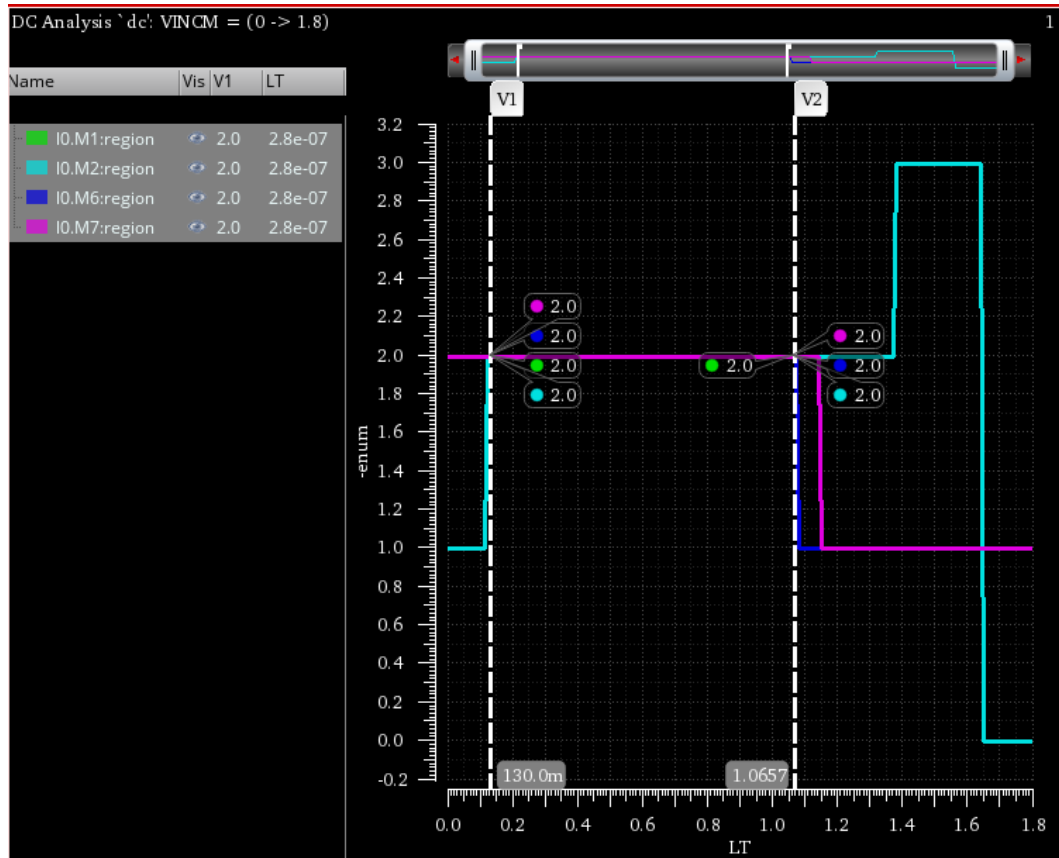
#### 4) CM large signal ccs (region vs VICM):




$$CMIR = 0.13:1.06$$

$$VINCM_{low} = -|VGS1| + |V * 1| + VGS3 = 0.153$$

$$VINCM_{High} = -|VGS1| - |Vdsat7| + VDD = 1.068$$


	Simulation	Calculation
VINCMmin	0.13v	0.153v
VINCMmax	1.06v	1.068v

 5) (Optional) CM large signal ccs (GBW vs VICM):



$$CMIR = 0.14:1.04$$

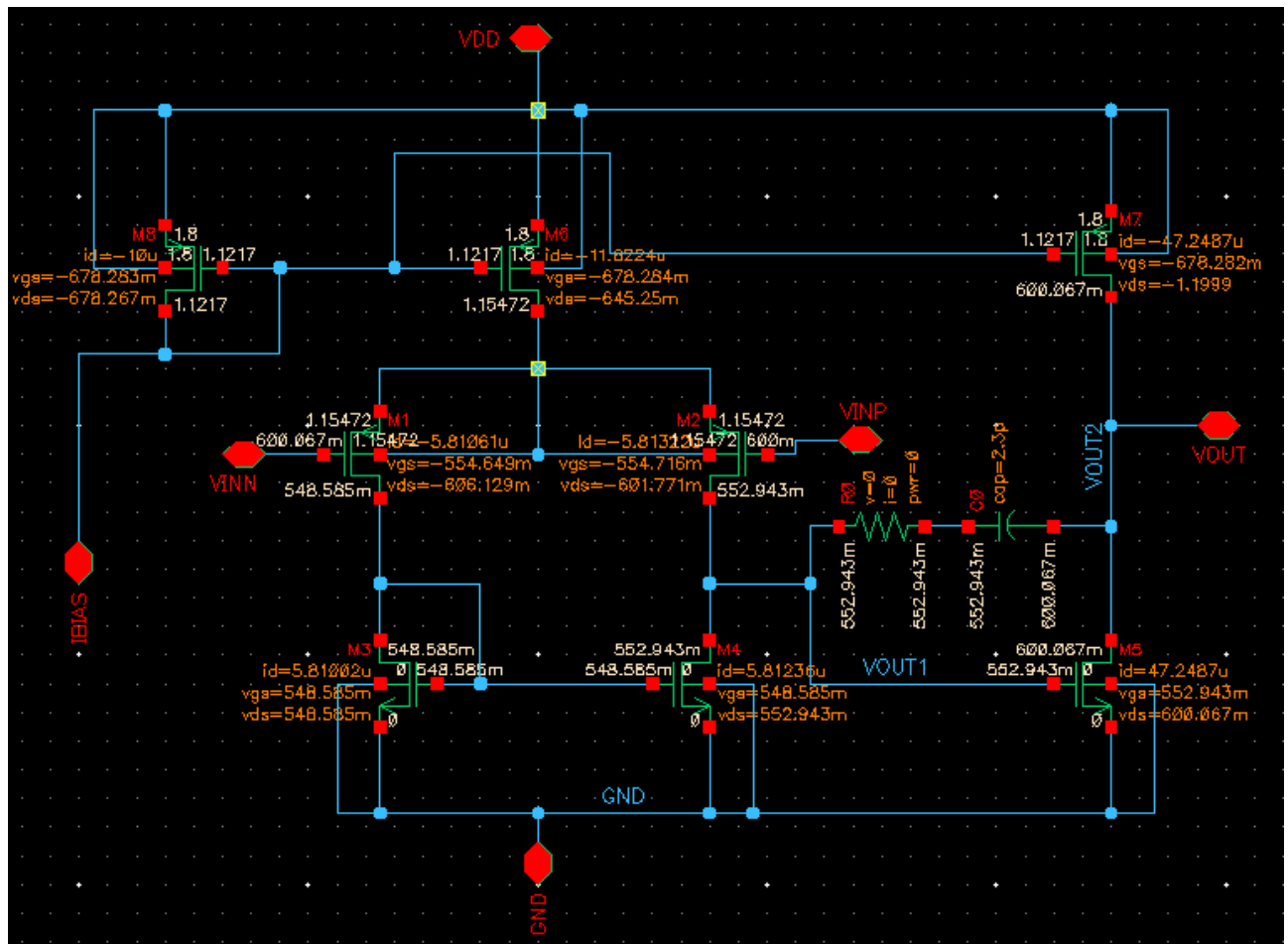1) Schematic of the OTA and the bias circuit with DC OP point clearly annotated in unity gain buffer configuration




-DC Voltages at the input terminals of the op amp aren't exactly equal because in closed-loop, the output will follow the input. The output voltage deviates from its CM level (the voltage at the mirror node for the 5T OTA Miller) in order to match the input voltage. Since the gain is finite, that will cause Verr between terminals of the op amp that causes the small deviation

-Vout1(open loop) =548.59mv, Vout1(closed loop) =552.94mv, they aren't exactly equal due to the feedback connection with a finite gain that causes Vout2 to deviate from its CM level to match the input terminal of the op amp, that also causes some deviation in Vout1 from its CM level.

- The current (and gm) in the input pair aren't exactly equal because in closed-loop OTA, the output will follow the input. The output voltage deviates from its CM level in order to match the input voltage. Since the gain is finite, that will cause a small imbalance in the circuit that act as a mismatch.

## 2) Loop gain:

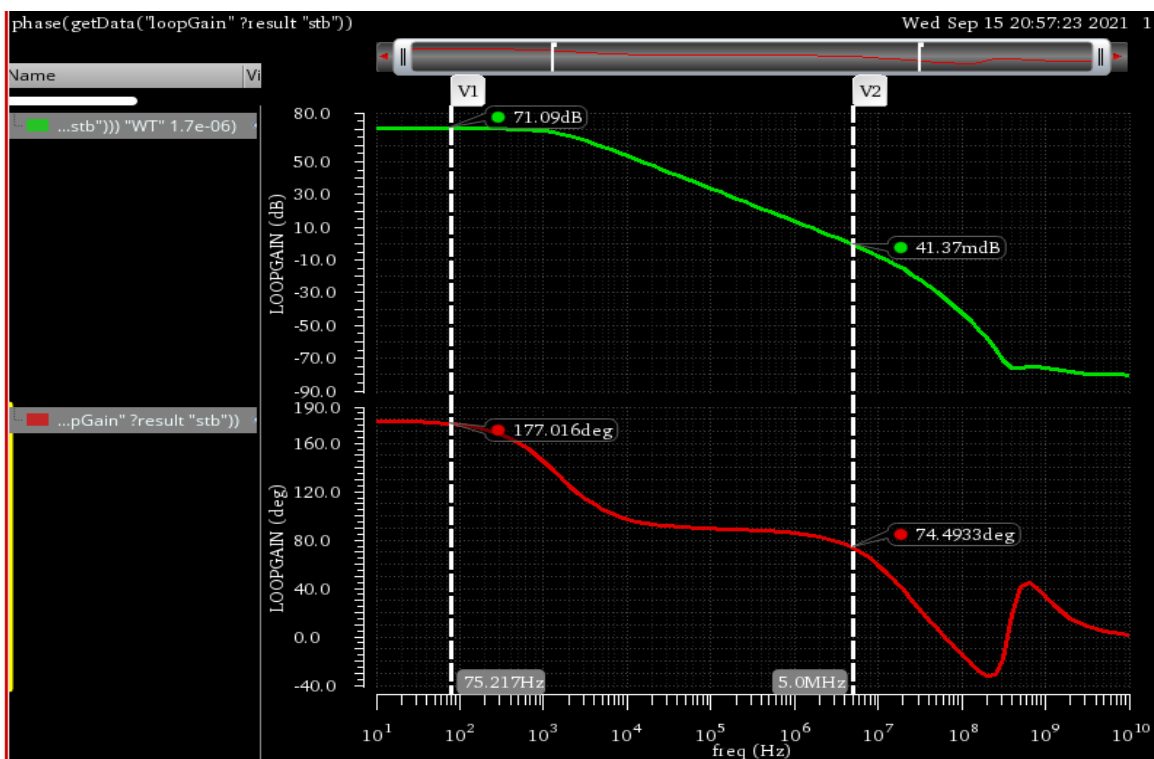

	Output	Nominal	Spec
VOUT			
dB20(mag(getData("loopGai...			
getData("/phaseMargin" ?res...	74.11		
ymax(mag(getData("loopGai...	3.278k		
unityGainFreq(mag(getData(...	5.133M		
gainBwProd(mag(getData("l...	5.285M		

Comparing DC gain and GBW with those obtained from open-loop simulation:

	Open-Loop	Loop gain
DC gain	68dB	71dB
Wu	5.161M	5.133M
GBW	5.3M	5.28M

Comment:



-We can notice that feedback with unity gain correction ( $B=1$ ) gives a loop gain equal to the open loop gain and doesn't affect GBW.

-Report PM. Compare with hand calculations. Comment:

$$W_u = \frac{gm1}{C_c} = 33.79MHz$$

$$W_{p2} = \frac{gm5}{C_l} = 129.48$$

$$PM = 90 - \tan^{-1} \frac{W_u}{W_{p2}} = 75.7$$

	Output	Nominal	
I	VOUT		
I	dB20(mag(getData("loopGai...		
I	getData("/phaseMargin" ?res...	74.11	

Comment:

-We assumed that  $W_{p2}=4W_u$  and that gives  $PM=76$  but we use  $C_c=2.3pf$  that reduce  $W_u$   
 -Results are almost equal.

Hand analysis:


$$LG = BA_{ol} = A_{ol} = 68.5dB$$

$$GBW = UGF = LG * BW = LG * W_{pout} = 5.5M$$

	Simulation	analysis
DC gain	71dB	68.5dB
Wu	5.133M	5.5M
GBW	5.28M	5.5M

### 3) Slew rate:

Report Vin and Vout overlaid

 

VOUT		
Vin		
slewRate(VT("VOUT") 0.25 ni...	4.666M	


$$\text{Slew rate} = \frac{IB1}{Cc} = \frac{11.62\mu A}{2.3pf} = 5.05Mv/s$$

	Simulation	Analysis
Slew rate	4.66M	5.05M

Comment:

-I don't exactly know why the deviation between the two results, maybe we neglect parasitic capacitances that shunts Cc or some thing else. **May be TA tells us at a comment or at WhatsApp.**

#### 4) Settling time:

 

Output	Nominal
/VOUT	
/Vin	
riseTime(VT("/VOUT")) 0.6 nil ...	52.03n

$$trise = 2.2taw = \frac{2.2}{Wu} = \frac{2.2}{33.79M} = 65.1n$$

	Simulation	Analysis
Rise time	52.03n	65.1n

Comment:

-The deviation may be due to the approximate expression of UGF.

-Actually there is a very small ringing that we have  $PM = 74 < 76$  in this case causes this small ringing.